



0.5V VLSI Processor Circuit Technologies

Sadaaki Hattori

Sakurai Laboratory

**Department of Electronic Engineering,
The University of Tokyo**


Contents



 
- 1. Background**
- 2. Circuit design at low voltage**
- 3. Low voltage logic technologies**
- 4. Low voltage SRAM memory cells**
- 5. Summary**

Trend of processor power

(Power consumption of processors published in ISSCC)




Power Crisis in VLSI processor

 

(ITRS: International Technology Roadmap for Semiconductors 1999)

174W Power in 2011 acceptable?

Contents

 

1. Background

2. Circuit design at low voltage

3. Low voltage logic technologies

4. Low voltage SRAM memory cell



5. Summary

Power & Delay Dependence on V_{DD} & V_{TH}

$$P = P_t f_{CLK} C_L V_{DD}^2 + \text{Leak power}$$

$$t_{pd} = \frac{k C_L V_{DD}}{(V_{DD} - V_{TH})^\alpha}$$

($\alpha=1.3$)

  

Contents



1. Background
2. Circuit design at low voltage
3. Low voltage logic technologies

Controlling V_{DD} and V_{TH} for low power


4. Low voltage SRAM memory cell
5. Summary

Controlling V_{DD} and V_{TH} for low power



	Active Power	Standby Power
Multiple V_{TH}	Dual- V_{TH}	MTCMOS SCCMOS BGMOS
Variable V_{TH}	VTCMOS	VTCMOS
Multiple V_{DD}	Dual- V_{DD}	(SCCMOS) (BGMOS)
Variable V_{DD}	Variable Supply	

Multi-Threshold CMOS (MTCMOS)

 

Benefits


- Low leakage current in standby

→ Reduced by 3 or 4 orders of magnitude.

Issues

- Large leak cut-off transistor
- Difficult for ultra low voltage
- Need for special Flip Flop


Super Cut-Off CMOS (SCCMOS)

 

V_{DD} can be decreased to 0.5V

V_{TH} can be decreased to less than 0.2V

Delay characteristics

 

SCCMOS

0.2V V_{TH} circuit
with 0.2V V_{TH}
cut-off MOSFET

MTCMOS

0.2V V_{TH} circuit
with 0.6V V_{TH}
cut-off MOSFET

Conventional

All 0.6V circuit
No cut-off
MOSFET


Standby current = 1pA

Controlling V_{DD} and V_{TH} for low power



	Active Power	Standby Power
Multiple V_{TH}	Dual- V_{TH}	MTCMOS SCCMOS BGMOS
Variable V_{TH}	VTCMOS	VTCMOS
Multiple V_{DD}	Dual- V_{DD}	(SCCMOS) (BGMOS)
Variable V_{DD}	Variable Supply	

Dual-Threshold Voltage technique

 

—— Critical paths ® Low- V_{TH} MOS
® High leakage, High speed


—— Non-critical paths ® High- V_{TH} MOS
® Low leakage, Low speed


Controlling V_{DD} and V_{TH} for low power




	Active Power	Standby Power
Multiple V_{TH}	Dual- V_{TH}	MTCMOS SCCMOS BGMOS
Variable V_{TH}	VTCMOS	VTCMOS
Multiple V_{DD}	Dual- V_{DD}	(SCCMOS) (BGMOS)
Variable V_{DD}	Variable Supply	

Dual Supply Voltage scheme

 

  Critical paths ® High- V_{DD} ® High speed

  Non-critical paths ® Low- V_{DD} ® Low power


Needs high speed level converter.

Controlling V_{DD} and V_{TH} for low power



	Active Power	Standby Power
Multiple V_{TH}	Dual- V_{TH}	MTCMOS SCCMOS BGMOS
Variable V_{TH}	VTCMOS	VTCMOS
Multiple V_{DD}	Dual- V_{DD}	(SCCMOS) (BGMOS)
Variable V_{DD}	Variable Supply	

Variable Supply Voltage scheme (VS)

 

Contents



1. Background
2. Circuit design at low voltage
3. Low voltage logic technologies


4. Low voltage SRAM memory cell

Memory in processor requires high speed

 5. Summary


Low voltage SRAM memory cells

Lowering V_{DD} of SRAM cell is difficult.



Leak → Data will be lost.

0.5-1V V_{DD} SRAM

 

$V_{DD}=0.5V$

High- $V_{TH}=0.35V$

Low- $V_{TH}=0.15V$

- Write-port and Read-port are divided in order to cut read error.
- Precharge level of Bit line is low because of leakage at low- V_{TH} MOS.

Low precharge → Low speed

High- $V_{TH}=0.35V$ → Low reliability

Summary

Low power technologies will be most important technologies for future VLSI processor.

- **Low voltage logic technologies**

	Active Power	Standby Power
Multiple V_{TH}	Dual- V_{TH}	MTCMOS, SCCMOS
Variable V_{TH}		
Multiple V_{DD}	Dual- V_{DD}	(SCCMOS)
Variable V_{DD}	Variable Supply	

- **Low voltage SRAM memory cell**

Future VLSI processor

