



Low-Power High-Speed SRAM Circuits using Low-Swing Bit-Lines

Sadaaki Hattori

Sakurai Laboratory


**Department of Electronic Engineering,
The University of Tokyo**

Contents



- 1. Background**
- 2. Low power logic technologies**
- 3. Low power SRAM technologies**
- 4. Summary**

Power crisis in VLSI processor

 

(ITRS: International Technology Roadmap for Semiconductors 1999)

174W Power in 2011 acceptable?

Contents



1. Background

2. Low-power logic technologies

3. Low-power SRAM technologies



4. Summary

Power & delay dependence on V_{DD} & V_{TH}

$$P = P_t f_{CLK} C_L V_{DD}^2 + \text{Leak power}$$

$$t_{pd} = \frac{k C_L V_{DD}}{(V_{DD} - V_{TH})^\alpha}$$

($\alpha=1.3$)

  


Contents



 
- 1. Background**
- 2. Low-power logic technologies**
- 3. Low-power SRAM technologies**
- 4. Summary**

Low voltage SRAM memory cell

Lowering V_{DD} of SRAM cell is difficult.



0.5-1V V_{DD} SRAM

 

$V_{DD}=0.5V$

High- $V_{TH}=0.35V$

Low- $V_{TH}=0.15V$



- Write-port and Read-port are divided in order to cut read error.
- Precharge level of Bit line is lower because of leakage at low- V_{TH} MOS.

Low precharge → Low speed


High- $V_{TH}=0.35V$ → Leakage

(Takakuni Douseki et al., "A 0.5V-1V MTCMOS/SIMOX SRAM Macro with Multi- V_{th} Memory Cells", IEEE International SOI Conference, Oct., 2000)


Conventional SRAM

  

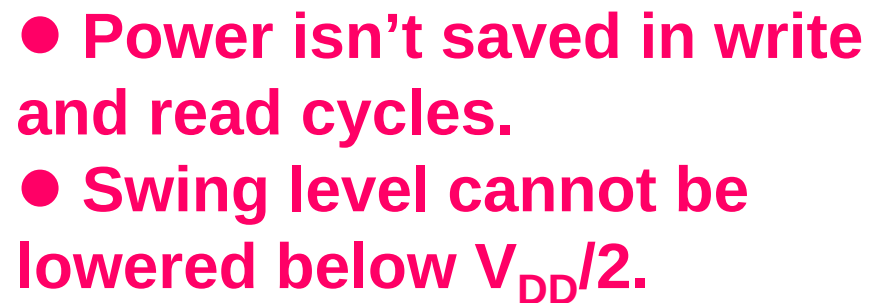Large capacitance
→ Large power at
precharge




10

 

- Can be lowered below $V_{DD}/2$.




Simulation result of energy consumption

 


Layout pattern of SRAM cells


Technology	0.35μm CMOS 3-metal (Rohm)
Organization	256 × 256 cells
Supply voltage	1.5V~2.5V
Core size	4.0mm ²
Cell size	55.3μm ²

 


Evaluation of read delay

 


Simulation result of cell read delay

 


Analysis of static noise margin

 

 
$$\beta = \frac{\beta_{\text{switch}}}{\beta_{\text{access}}}$$




Simulation result of static noise margin

 

Input-output characteristic of inverters

 


Layout pattern of 4 cells

 

11% large area

An SRAM architecture

 


Logic
 $V_{DD}=0.5V$




High speed
level converter
is needed.

Memory
 $V_{DD}=1.0V \sim 1.5V$

 


Level converters (0.5V → 1.0V)

Conventional

 

 
V_{DDH} : High V_{DD}
 V_{DDL} : Low V_{DD}



Rising delay : 1ns
Falling delay : 1ns

Level converters (0.5V → 1.0V)


Proposed

 

Falling delay : 0.4ns

Power increase

Proposed (Inverter type)

 

Rising delay : 0.6ns

Power increase

Summary



Power crisis in VLSI processor

- **Low-power logic technologies**
- **Low-power SRAM technologies**

Low-swing bit line

80% power saving at $V_{DD}=1.5V$

11% area increase

5% delay increase at $V_{DD}=1.5V$

Logic : Low- V_{DD}

Memory : High- V_{DD}

→ **Needs high-speed level converter.**

Future works



Improvement of design

- Area
 - Improvement of layout
- Delay
 - High-speed level converter

Logic design

Decoder, buffer, control

Measurement

- Characteristic
- Power
- Delay



**Low-power High-speed SRAM circuit
as a memory for 0.5V 1GHz processor**